

Circuit for protecting low-voltage SAR ADC from electrical overstress with minimal impact on performance

Dale Li


Single-Ended Input ($V_{REF} = +5V$)	ADC Input	Digital Output ADS8860
$V_{inMax} = +5V$	$AINP = +5V, AINN = 0V$	$FFFF_H$
$V_{inMin} = 0V$	$AINP = 0V, AINN = 0V$	0000_H

Power Supplies and Reference			
Vcc on OPA828	Vee on OPA828	Clamp Voltage and Reference	ADS8860 AVDD and DVDD
+12V	-12V	+5V	+3V

Design Description

This cookbook circuit describes how to connect a high-voltage amplifier (for example, $\pm 12V$) to a low voltage ADC (for example, 0V to 5V) and clamp the output voltage of the amplifier to protect the ADC from electrical overstress damage. Furthermore, this document shows the impact that the protection clamp has on system performance. This circuit is useful in [test and measurement](#), and [factory automation and control](#).

This example circuit connects the [OPA828](#) to the [ADS8860](#). The OPA828 device has $\pm 12V$ supplies and the ADS8860 device has 0-V to 5-V input range. Normally, the amplifier supplies are matched to the ADC input range to prevent overstress of the inputs, but in some cases it may be useful to connect a higher voltage amplifier to a low-voltage ADC. Under a fault condition, when the output of the amplifier is above 5V or below ground, the diodes D1 and D2 turn on and limit the ADC input voltage to safe levels. The resistor R_p limits the output current under fault conditions. The R_p resistor is connected inside the amplifier feedback so that the impedance is reduced by the amplifiers feedback, under normal conditions. Keeping R_p in the feedback improves AC system performance (SNR and THD). This protection method is suitable for other precision SAR ADC with a switched capacitor input.

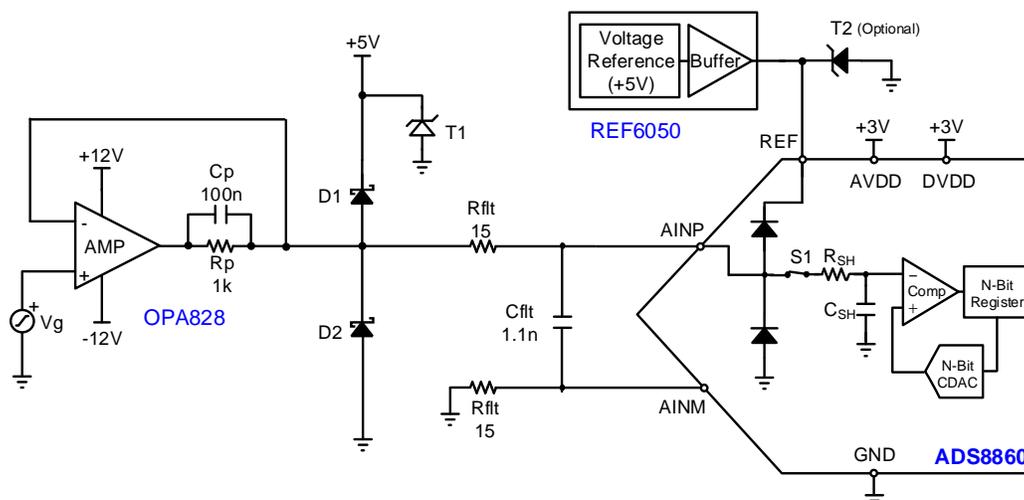

Specifications

Specification	Goal	Calculated	Simulated	Measured
Transient Settling Error	< 1/2LSB (< 38.15 μ V)		0.3 LSB (23.1 μ V)	
THD	< -108dB			-113.7dB
SNR	> 92dB			93.3dB
Bandwidth	> 1MHz	4.82MHz	5.08MHz	
Noise	< 1/2LSB (< 38.15 μ V)	11.3 μ V _{RMS}	10.04 μ V _{RMS}	

Design Notes

1. The BAT54 diode is selected for D1 and D2 because of its lower forward voltage, low leakage current, and low capacitance as the capacitance on the diode is nonlinear and can introduce distortion.
2. The OPA828 device is a high bandwidth (45MHz) precision amplifier which is good enough to drive the 16-bit precision SAR ADC ADS8860 device. See the *TI Precision Labs – ADCs* training video: [Introduction of Selecting and Verifying the Driver Amplifier](#), for details.
3. Select the COG type capacitor for C_{fit} to minimize the distortion.

Component Selection

- The following table lists the maximum output voltage and current for the OPA828 amplifier. The table also lists the absolute maximum specifications for the ADS8860 ADC. The ADC input voltage range is set as the maximum voltage before turning on the internal ESD diodes. The input current range is the maximum current the internal ESD diodes can support continuously.

OPA828 Output		ADS8860 Absolute Maximum Ratings		
OPA828 maximum output voltage: (EOS voltage range - V_o)	$-12V \leq V_o < 0V$	AINP or AINN to GND	-0.3V	$V_{ADC_in_min}$
	$+5V < V_o \leq +12V$		+5.3V	$V_{ADC_in_max}$
OPA828 maximum output current: (Short-circuit current - I_{sc})	-50mA	Input current	-10mA	$I_{ADC_in_min}$
	+50mA		+10mA	$I_{ADC_in_max}$

- Select a diode with a low forward drop, low leakage current, sufficient forward current, and low capacitance. Generally, a Schottky diode is used for its low forward drop. See the video series on [EOS Protection for ADCs](#) for details on selection of the diode and other information on overstress protection. In this example, the BAT54 Schottky diode is selected as it has a good forward voltage drop as well reasonable leakage current and capacitance. The BAT54 is a common choice for EOS protection.
- For this circuit, a -12-V output from the OPA828 amplifier is limited to -0.42V, and a 12-V output is limited to 5.42V. The largest voltage across R_p occurs when the amplifier output is at -12V. Hence, R_p is determined by the following equation:

$$R_p > \frac{V_{fD2} - V_{oNegMax}}{I_{fault}} = \frac{-0.42V - (-12V)}{15mA} > 772\Omega \text{ (round up to } 1k\Omega)$$

- In the following equation, the fault current and power dissipated is calculated in R_p during an electrical overstress fault event. The objective is to make sure that the correct power rating is used on the resistor R_p .

$$I_{fault} = \frac{V_{fD2} - V_{oNegMax}}{R_p} = \frac{-0.42V - (-12V)}{1k\Omega} = 11.6mA$$

$$P_{Rp} = (I_{fault})^2 R_p = (11.6mA)^2 (1k\Omega) = 134mW \text{ (use } 0.2W \text{ for margin)}$$

- The resistor R_{flt} acts as a charge bucket filter and also to limit the current under a fault condition. First, a minimum value of R_{flt} is determined for fault protection by assuming D2 has a 0.42-V drop on it and the internal ESD diode has 0.3V on it. Using this voltage and the absolute maximum input current rating, the minimum value of R_{flt} for current limiting is selected (12 Ω).


$$R_{flt} > \frac{V_{ADC_in_min} - V_{fD2}}{I_{ADC_in_max}} = \frac{-0.3V - (-0.42V)}{10mA} > 12\Omega$$

- Next, a [TINA SPICE](#) optimization is performed on R_{flt} and C_{flt} to get the best settling. For this optimization the minimum value of R_{flt} is set to 12 Ω for input protection (see step 5). The final value for the (15 Ω) and (1.1nF) in the charge bucket circuit are optimized and selected for the best signal settling and AC performance. See the methods described in [SAR ADC Front-End Component Selection](#) for details.
- The capacitor C_p in parallel with R_p is used to reduce the AC impedance of the protection network ($R_p || C_p$) at higher frequencies. This value may impact the stability of the design as well. The idea is to set the cutoff frequency of the network to be much lower than the amplifier cutoff. The exact value may not be very critical so here we round to a common standard value of 100nF. Also, note that we confirm stability later in this document.

$$C_p \approx \frac{1}{2\pi R_p f} = \frac{1}{2\pi (1k\Omega)(1kHz)} > 159nF \text{ (choose } 100nF \text{ and check stability)}$$

DC Transfer Characteristics


The following graph shows a linear output response for inputs from single-ended -40V to $+40\text{V}$. See [Determining a SAR ADC's Linear Range when using Operational Amplifiers](#) for detailed theory on this subject. Note that the output range is intentionally limited to -0.42V to 5.38V using Schottky diodes to protect the ADS8860 device. Note that Schottky diodes are used because the low forward voltage drop (typically less than 0.3V) keeps the output limit very near the ADC supply voltages. The absolute maximum rating for the ADS8860 is $-0.3\text{V} < V_{in} < \text{REF} + 0.3\text{V}$.

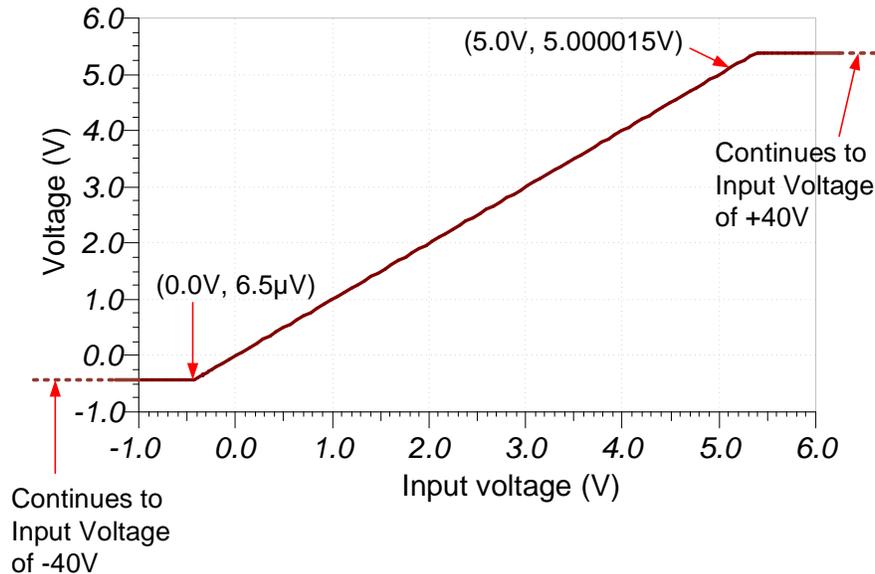

AC Transfer Characteristics


The bandwidth for this circuit is limited by the RC charge bucket circuit (R_{filt} and C_{filt}). The hand calculation and the simulated results compare well (hand calculation $f_c = 4.82\text{MHz}$, simulated $f_c = 5.08\text{MHz}$). See the [Op Amp Bandwidth](#) video series for more details on this subject.
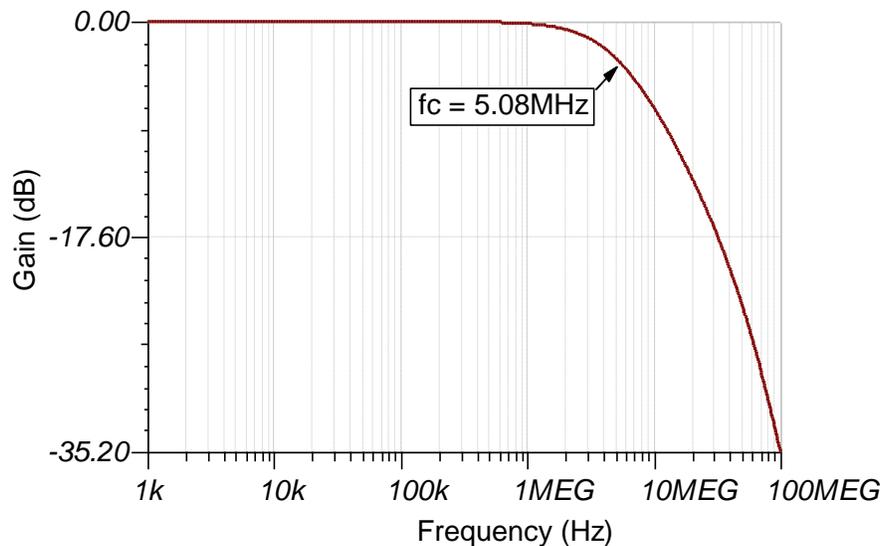
$$f_c = \frac{1}{2\pi \cdot (2 \cdot 15\Omega) \cdot (1.1\text{nF})} = 4.82\text{MHz}$$



Transient ADC Input Settling Simulation

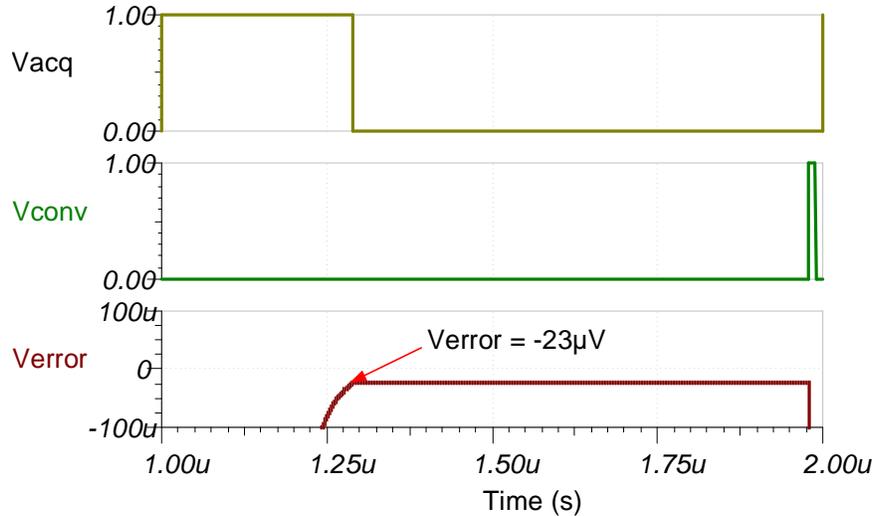The following simulation shows settling to a +5-V DC input signal with the OPA828 device. This type of simulation shows that the sample and hold kickback circuit is properly selected to drive ADS8860 at a 1-MSPS sampling rate and meets the desired ½ of a LSB (38.15µV). See the [Introduction to SAR ADC Front-End Component Selection](#) for detailed theory on this subject.




Noise Simulation

In this circuit example, the noise is dominated by the wide band amplifier noise so the resistors do not contribute significantly. Hence, the noise from the resistors is neglected in this calculation:

$$E_n = e_{n_{828}} \cdot \sqrt{K_n \cdot f_c}$$


$$E_n = 4\text{nV} / \sqrt{\text{Hz}} \cdot \sqrt{1.57 \cdot 5.08\text{MHz}} = 11.3\mu\text{V}_{\text{RMS}}$$

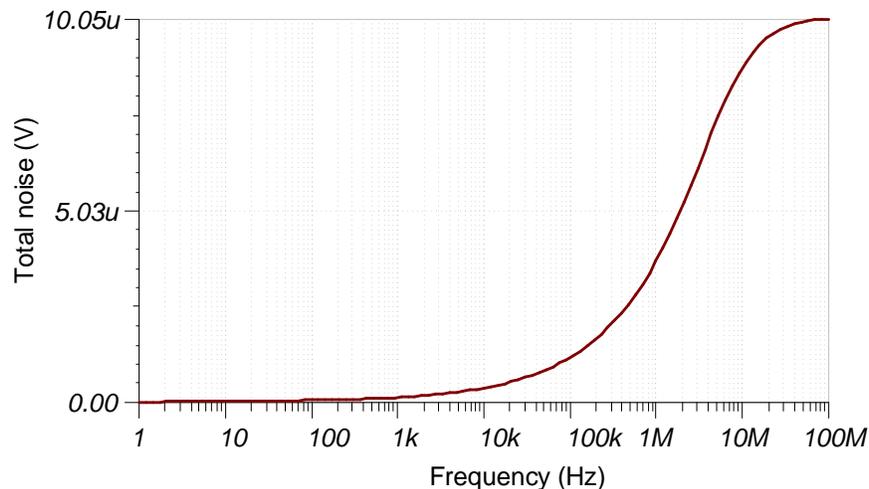Note that calculated and simulated match well (simulated = 10.05µV_{RMS} as in the following graph). See [Amplifier Noise Simulations \(Op Amps: Noise 5\)](#) for detailed theory on amplifier noise calculations, and [Calculating the Total Noise for ADC Systems](#) for data converter noise.




Stability

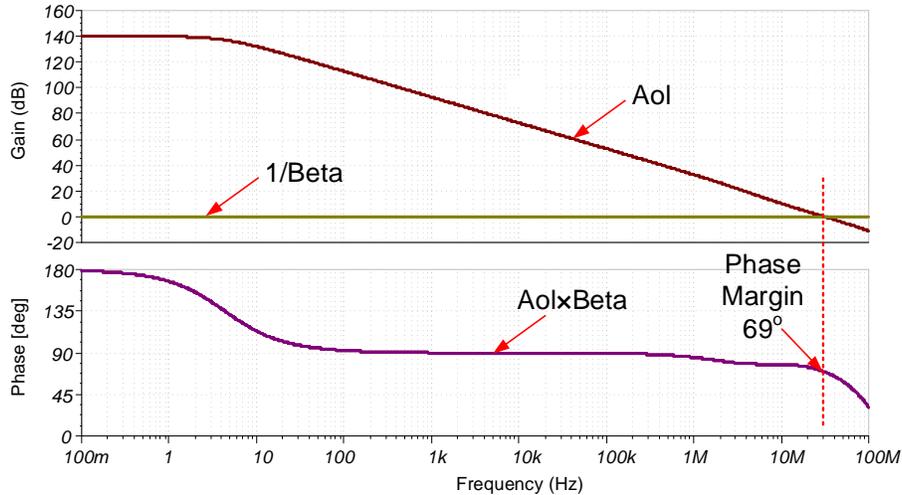The following simulation shows a stability check for the performance-improved solution previously shown. This design has 69 degrees of phase margin which indicates that the circuit is very stable. Generally, the circuit which has more than 45 degrees of phase margin is considered to be stable. For more information on stability analysis check the [Op Amps: Stability](#) video series.



AC Performance Checked on Hardware

The following spectral analysis is measured using the [Precision Labs EVM \(PLABS-SAR-EVM-PDK\)](#). The AC performance including all the protection circuitry is better than the typical specifications in the [ADS8860 16-bit, 1-MSPS, Serial Interface, Micropower, Miniature, Single-Ended Input, SAR Analog-to-Digital Converter data sheet](#) (Measured SNR = 93.3dB, THD = -113.7dB, ADS8860 Typical: SNR = 92dB, THD = -108dB).

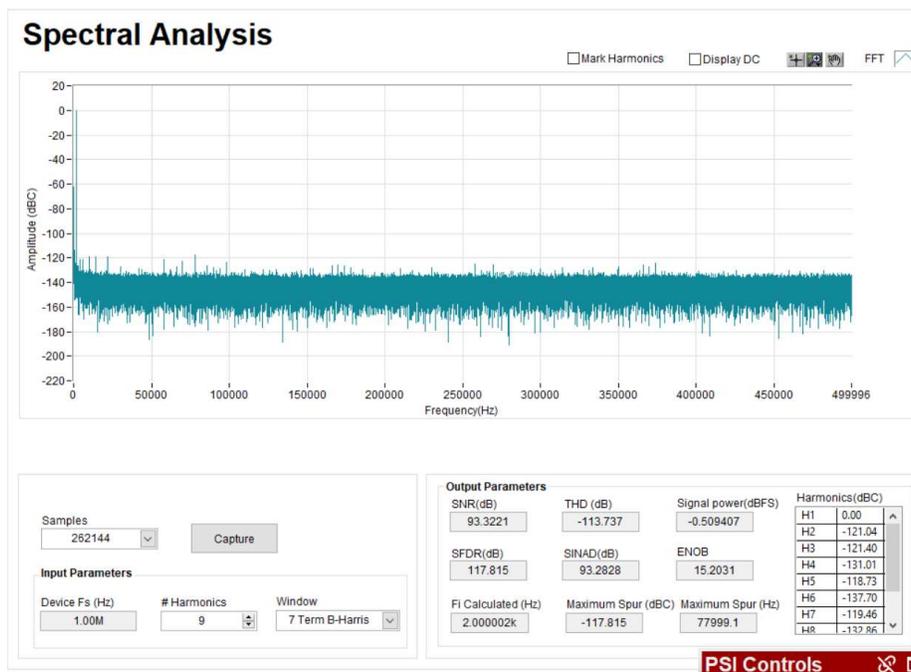

Design Featured Devices and Alternative Parts

Device	Key Features	Link	Other Possible Devices
ADS8860	16-bit resolution, 1-MSPS sample rate, single-ended input, V_{REF} input range 2.5V to 5.0V, SPI, SAR ADC	http://www.ti.com/product/ADS8860	http://www.ti.com/adcs
ADS9224R	16-bit, 3-MSPS, dual-channel, simultaneous-sampling SAR ADC with internal reference and enhanced SPI, SAR ADC	http://www.ti.com/product/ADS9224R	http://www.ti.com/adcs
ADS8168	16-bit, 1-MSPS, 8-channel, SAR ADC with V_{REF} , V_{REF} buffer and multiplexer, enhanced SPI SAR ADC	http://www.ti.com/product/ADS8168	http://www.ti.com/adcs
OPA828	36-V, high-precision, low-noise, low-bias current, JFET- input operational amplifier	http://www.ti.com/product/OPA828	http://www.ti.com/opamps

Link to Key Files

TINA source files – <http://www.ti.com/lit/zip/SBAC249>.

Other References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated